

2022100124 권서은

## 1. RCA 16


b) The critical path is Cin -> Cout.

If we look at the 16-bit adder, the input signals to adders are a, b and cin, and the output signals are s and cout.


If we look at the waveform, the time when c[15], the last node of cout, becomes 1 is 3566ps, and the time when cin\_q becomes 1 is 3070ps. Since c[15] is the last node of cout, the delay from cin\_q to cout is 496ps.

However, if we consider Cin -> S, we have to see the delay from cin\_q to s\_w[15], the last node of S. The time when s\_w[15] becomes 1 is 3545ps, and the time when cin\_q becomes 1 is 3070ps. So the delay from cin\_q to s\_w[15] is 475ps.

c)

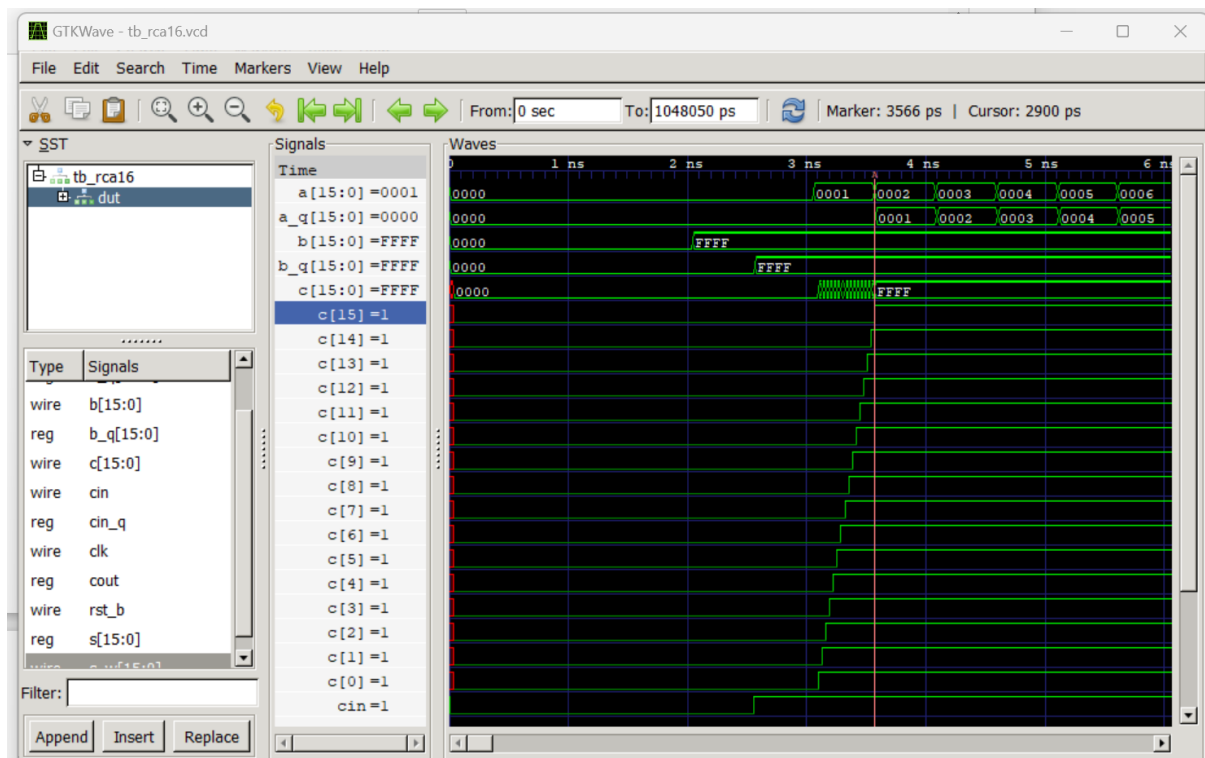

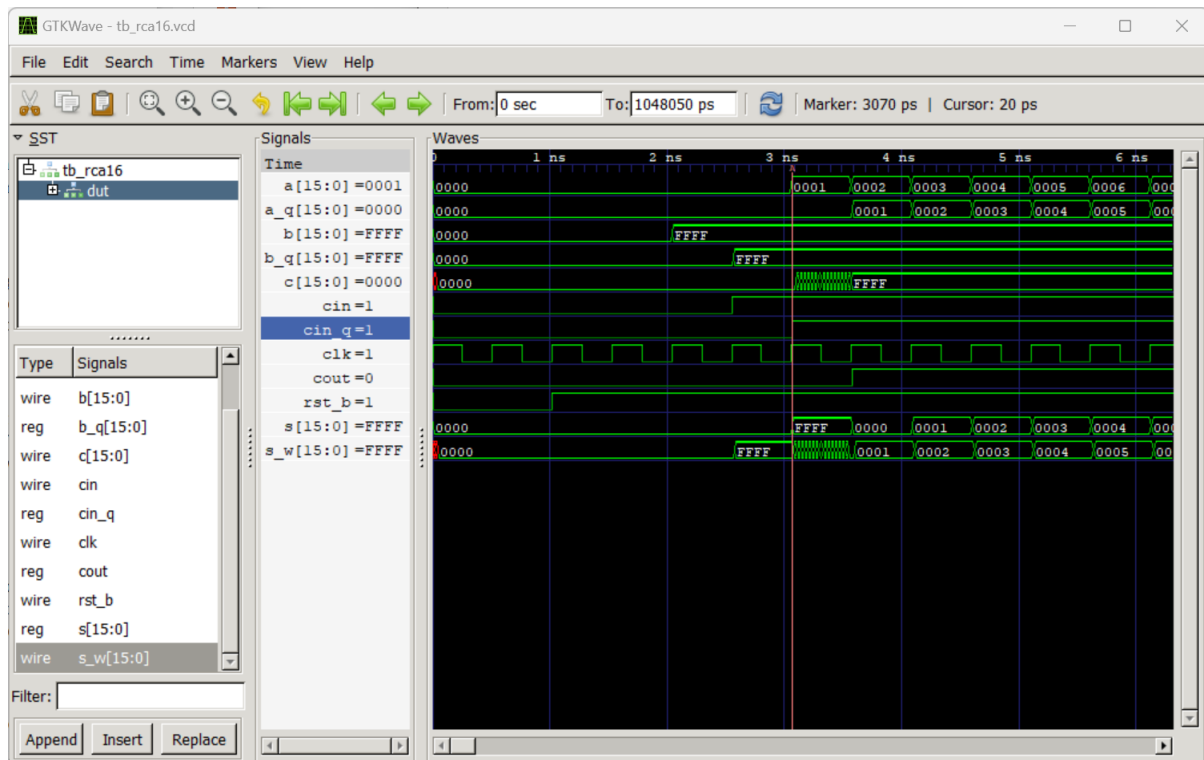This is the marker line when c[15], the last node of cout, changes from 1'b0 to 1'b1. The location (time) of a marker is 3566ps.



This is the marker line when cin\_q changes from 0 to 1. The location (time) of a marker is 3070ps.

Since  $3566\text{ps} - 3070\text{ps}$  is  $496\text{ps}$ , the delay of the critical path in the RCA16 design is  $496\text{ps}$ .

d)

The shortest clock period that can generate correct result is 510 ps, since the delay of the critical path is 496ps, and the  $t_{pcq}$  of D flip-flop is 10ps. If we add them together, it is 506ps, but since the clock periods should be figured out in 10ps resolution, we can say that the shortest clock period is 510ps.

## 2. CLA


b) The critical path is cin -> s.

If we look at the 16-bit adder, the input signals to adders are a, b and cin, and the output signals are s and cout.


If we look at the waveform, the time when c[3], the last node of cout, becomes 1 is 1030ps, and the time when cin\_q becomes 1 is 910ps. Since c[3] is the last node of cout, the delay from cin\_q to cout is 120ps.

However, if we consider Cin -> S, we have to see the delay from cin\_q to s\_w[15], the last node of S. The time when s\_w[15] becomes 1 is 1044ps, and the time when cin\_q becomes 1 is 910ps. So the delay from cin\_q to s\_w[15] is 134ps.

c)

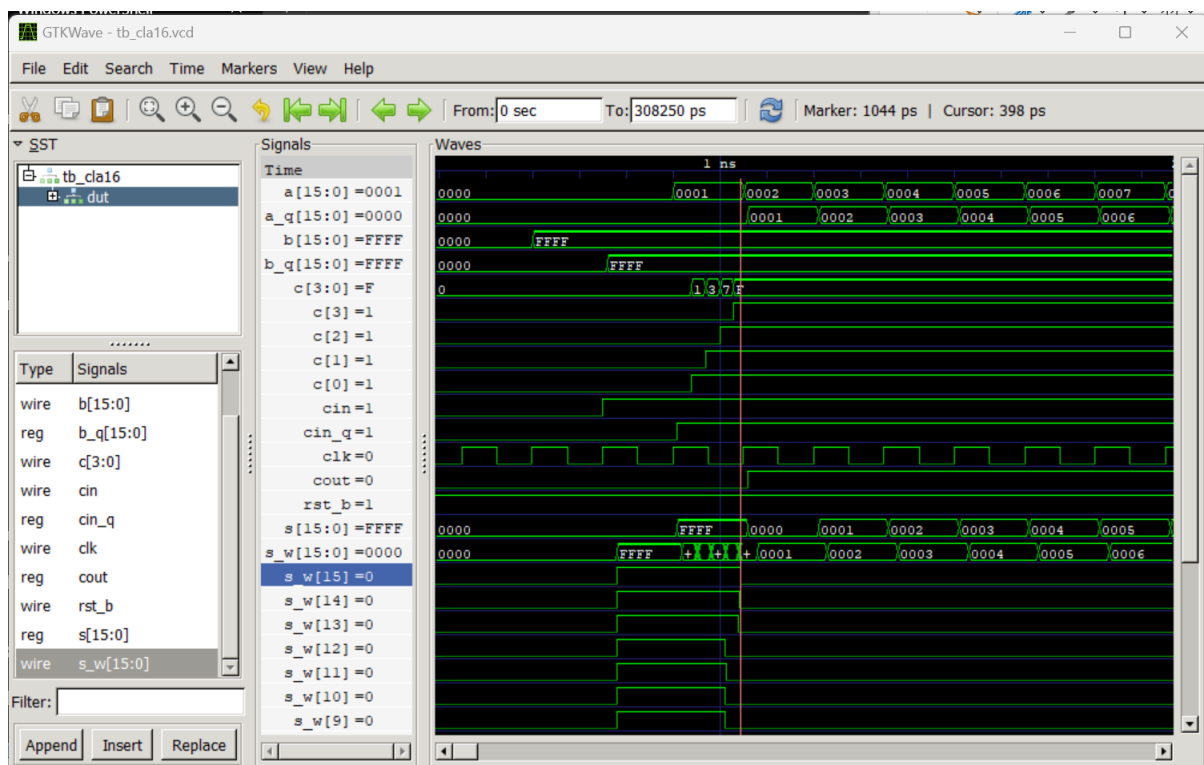

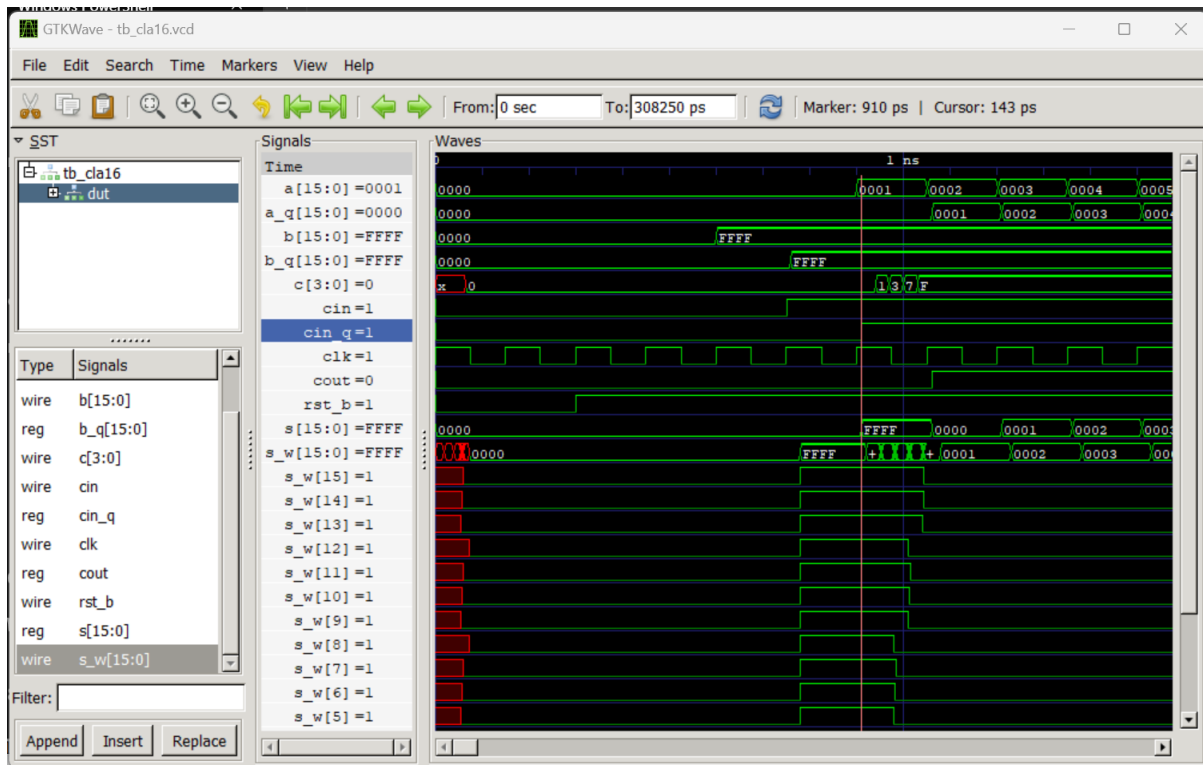This is the marker line when s\_w[15], the last node of s, changes from 1'b0 to 1'b1. The location (time) of a marker is 1044ps.



This is the marker line when cin\_q changes from 0 to 1. The location (time) of a marker is 910ps.

Since  $1044\text{ps} - 910\text{ps}$  is 134ps, the delay of the critical path in the CLA16 design is 134ps.

d)

The shortest clock period that can generate correct result is 150 ps, since the delay of the critical path is 134ps, and the  $t_{pcq}$  of D flip-flop is 10ps. If we add them together, it is 144ps, but since the clock periods should be figured out in 10ps resolution, we can say that the shortest clock period is 150ps.